

# Laboratory 8

## **UART Design (Part 2)**

Computer Architecture

A.Y. 2023/24


# Laboratory goals

- Understand the structure and functions of a UART device
- Design and implement said functions in VHDL (over multiple labs)
- In this lab: continue implementing the transmission logic.

# Recap
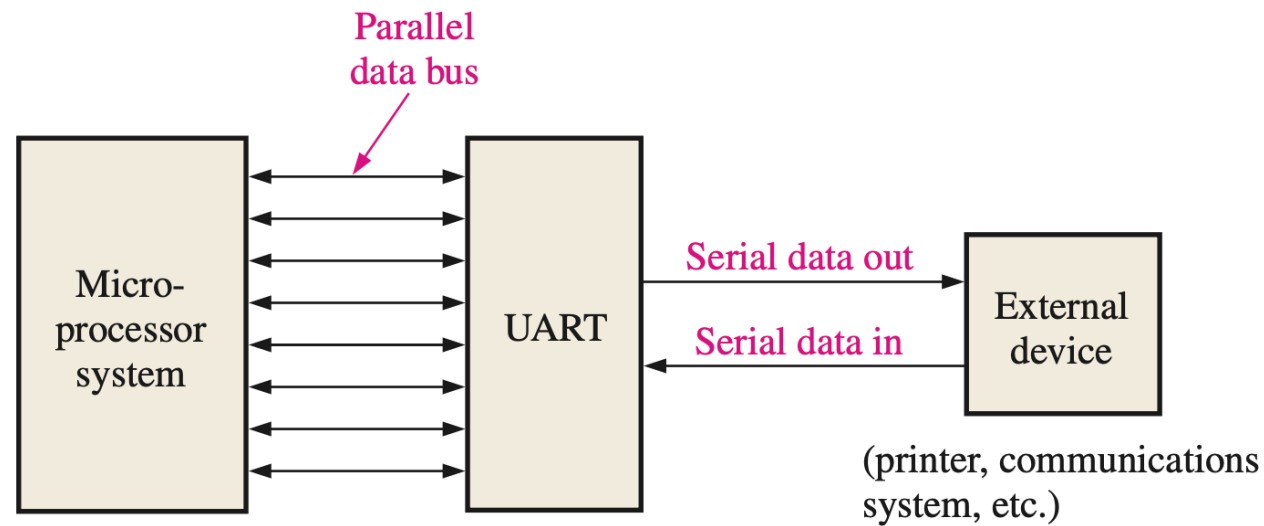
# UART – Definition


A Universal Asynchronous Receiver Transmitter (UART) device is used to communicate between a microprocessor, or device that uses parallel data buses, and devices that communicate in serial data.


 
# UART Data Transfer Protocol


To enable data transfer without synchronization, both the UART and the device at the other end must agree on:

- Transmission speed (i.e. bit rate or baud)
- Data format: send 8-bit characters, framed by a start bit and a stop bit.




# Design of a UART – Example

 1. *Essential block diagram for your design.*



# Design of a UART – Example

## 2. Finite State Machine diagram (TX).

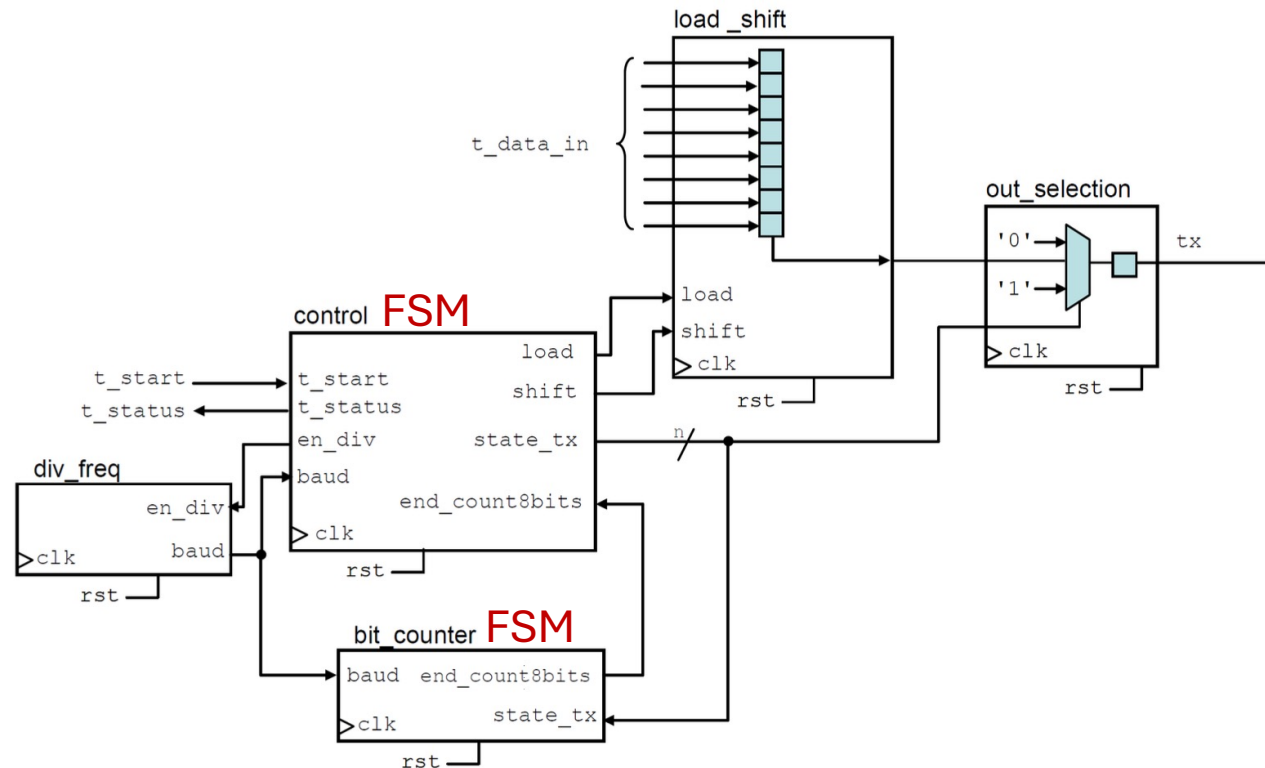

# Transmitter design

**Exercise 1:** Implement a shift register in VHDL and validate its functionality.

**Exercise 2:** Implement the frequency divider in VHDL and test its functionality.

*Ex. 2b:* If your design has other blocks, implement and test them in VHDL.

**Exercise 3:** Design the transmission control block FSM, define the number of states and the truth table.

**Exercise 4:** Implement the transmission control block in VHDL.

**Exercise 5:** Join all the blocks and design a testbed to validate the transmission functionality.



# Laboratory 7 Solution – Transmitter (part 1)

# Transmitter design – Solution (1)

**Exercise 1:** Implement a shift register in VHDL and validate its functionality.


```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY load_shift IS
    PORT( t_data_in : IN STD_LOGIC_VECTOR (7 downto 0);
          clk, load, shift, rst : IN STD_LOGIC;
          t_data_out : OUT STD_LOGIC);
END load_shift;

ARCHITECTURE behavior OF load_shift IS
    SIGNAL tmp_reg: STD_LOGIC_VECTOR (7 downto 0);
BEGIN
    PROCESS (rst,clk)
    BEGIN
        IF (rst = '1') THEN
            tmp_reg <= (OTHERS=>'0');
            t_data_out <= '0';
        ELSIF (clk'EVENT and clk = '1') THEN
            IF (load = '1') THEN
                tmp_reg <= t_data_in;
            ELSIF (shift = '1') THEN
                t_data_out <= tmp_reg(0);
                tmp_reg(0) <= tmp_reg(1);
                tmp_reg(1) <= tmp_reg(2);
                tmp_reg(2) <= tmp_reg(3);
                tmp_reg(3) <= tmp_reg(4);
                tmp_reg(4) <= tmp_reg(5);
                tmp_reg(5) <= tmp_reg(6);
                tmp_reg(6) <= tmp_reg(7);
            END IF;
        END IF;
    END PROCESS;
END behavior;
```

# Transmitter design – Solution (2)

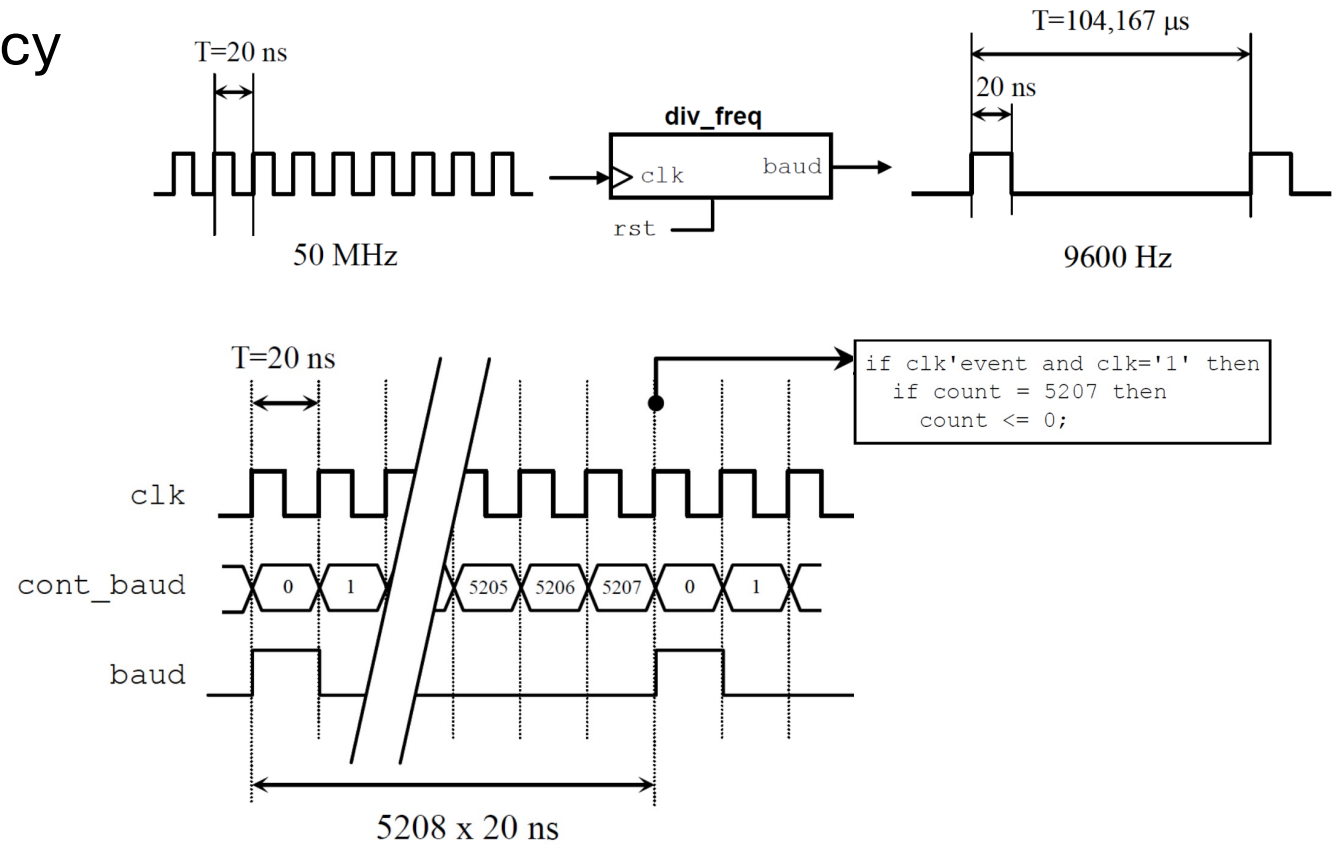**Exercise 2:** Implement the frequency divider in VHDL and test its functionality.



# Transmitter design – Solution (2)

**Exercise 2:** Implement the frequency divider in VHDL and test its functionality.

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY div_freq IS
    GENERIC (N: INTEGER := 10);
    PORT( clk, rst, en_div: IN STD_LOGIC;
          baud: OUT STD_LOGIC);
END div_freq;

ARCHITECTURE behavior OF div_freq IS
    SIGNAL count_baud: INTEGER RANGE 0 TO N := 0;
BEGIN
    PROCESS (clk, rst)
    BEGIN
        IF rst = '1' THEN
            baud <= '0';
            count_baud <= 0;
        ELSIF (clk'EVENT and clk = '1' and en_div = '1') THEN
            IF count_baud = N THEN
                count_baud <= 0;
                baud <= '1';
            ELSE
                count_baud <= count_baud + 1;
                baud <= '0';
            END IF;
        END IF;
    END PROCESS;
END behavior;
```

# Transmitter design – Solution (2b)

Ex. 2b: If your design has other blocks (**bit counter**), implement and test them in VHDL.


```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY bit_counter IS
    PORT( clk, baud, rst: IN STD_LOGIC;
          end_count8bits: OUT STD_LOGIC;
          state_tx: IN STD_LOGIC_VECTOR (1 downto 0));
END bit_counter;

ARCHITECTURE fsm OF bit_counter IS
    TYPE state IS (zero, one, two, three, four, five,
                  six, seven, eight);
    SIGNAL pr_state, nx_state: state;
    SIGNAL tmp: STD_LOGIC;
BEGIN
    seq:
    PROCESS (rst, clk)
    BEGIN
        IF (rst = '1') THEN
            end_count8bits <= '0';
            pr_state <= one;
        ELSIF (clk'EVENT AND clk = '1') THEN
            IF (baud = '1' and state_tx = "10") THEN
                end_count8bits <= tmp;
                pr_state <= nx_state;
            END IF;
        END IF;
    END PROCESS seq;
    comb:
    PROCESS(pr_state)
    BEGIN
        CASE pr_state IS
            WHEN zero =>
                tmp <= '0';
                nx_state <= one;
            WHEN one =>
                tmp <= '0';
                nx_state <= two;
            WHEN two =>
                nx_state <= three;
            WHEN three =>
                nx_state <= four;
            WHEN four =>
                nx_state <= five;
            WHEN five =>
                nx_state <= six;
            WHEN six =>
                nx_state <= seven;
            WHEN seven =>
                nx_state <= eight;
            WHEN eight =>
                nx_state <= zero;
                tmp <= '1';
        END CASE;
    END PROCESS comb;
END fsm;
```
 
# Transmitter design – Solution (2b)

Ex. 2b: If your design has other blocks (**out\_selection**), implement and test them in VHDL.




```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY out_selection IS
    PORT(
        clk, rst , in_data: IN STD_LOGIC;
        state_tx: IN STD_LOGIC_VECTOR (1 downto 0);
        tx: OUT STD_LOGIC);
END out_selection;

ARCHITECTURE behavior OF out_selection IS
BEGIN
    PROCESS(clk, rst)
    BEGIN
        IF (rst = '1') THEN
            tx <= '1';
        ELSIF (clk'EVENT and clk='1') THEN
            CASE state_tx IS
                WHEN "00" =>
                    tx <= '1';
                WHEN "01" =>
                    tx <= '0';
                WHEN "10" =>
                    tx <= in_data;
                WHEN "11" =>
                    tx <= '1';
            END CASE;
        END IF;
    END PROCESS;
END behavior;
```

# Transmitter design – Solution (3)

 **Exercise 3:** Design the transmission control FSM, define the number of states and the truth table.



**baud:** one clock pulse.

*Note:* rst signals and outputs are omitted in the graph, but should be considered (in the truth table.)

# Transmitter design – Solution (3)

**Exercise 3:** Design the transmission control block and the bit counter FSMs, define the number of states and their truth tables.

pr_state	Inputs			nx_state	Outputs			
	t_start	baud	end_count8bits		load	shift	en_div	t_status
t_init	0	X	X	t_init	0	0	0	0
t_init	1	X	X	t_bit_init	1	0	0	0
t_bit_init	X	0	X	t_bit_init	0	0	1	1
t_bit_init	X	1	X	t_bits_data	0	baud	1	1
t_bits_data	X	X	0	t_bits_data	0	baud	1	1
t_bits_data	X	X	1	t_bit_end	0	0	1	1
t_bit_end	X	0	X	t_bit_end	0	0	1	1
t_bit_end	X	1	X	t_init	0	0	1	1



# References

- Tokheim, R. Digital Electronics: Principles And Applications
- Floyd, Thomas L. Digital Fundamentals, 2016. Pearson
- Mano, Morris. Digital Desing.
- Intel QUARTUS Help Manuals
- Tocci, Ronald. Digital Systems Principles and Applications.